

EE101: Electrical & electronic circuits: week-1:

*pioneers:-

Siddarth P. duttagupta.

maxwell laws:-

no decision making.
large scale.
mechanical.
resistors
capacitors

Small Scale.
electron flow explanations.
- diodes - BJTs.

/ has decision making.

$$\vec{\nabla} \cdot \vec{E} = \frac{P}{\epsilon_0}$$

} Gauss law for electricity

$$\vec{\nabla} \cdot \vec{B} = 0$$

} Gauss law for magnetism

$$\vec{\nabla} \times \vec{E} = - \frac{\partial \vec{B}}{\partial t}$$

} Lens law | Faradays law.

$$\vec{\nabla} \times \vec{B} = \mu_0 \left(I + \epsilon_0 \cdot \frac{\partial \vec{E}}{\partial t} \right)$$

Ampères
loop law.

} maxwell corrected amperes law. part.

electronic

part;

controls electrical

part.

fast imp. discovery

in last 100 yrs...

electronic

part;

controls electrical

part.

→ magnetic properties:-

1) dia:- response opposes the applied \vec{B} .

$$\therefore \mu_r < 1$$

$$\text{Ex: Cu; } \mu_r = 0.9999980$$

2) para:- response aligns with applied \vec{B}

$$\therefore \mu_r \geq 1$$

$$\text{Ex: air; } \mu_r = 1.0000004$$

3) ferro: $\mu_r \gg 1$. Spontaneous magnetisation persists.

111111

Iron.

4) Antiferro: net is zero. (due to moment cancellation).

1V77V

5) Ferri: net is non-zero, but not as strong as Ferro.

1V777V

* Lorentz force:

$$\vec{F} = q(\vec{E} + \vec{v} \times \vec{B})$$

(same q/m ; can't separate via mass spectroscopy)

Biot-Savart law:



$$\vec{B} = \frac{\mu_0}{4\pi} \cdot i \frac{d\vec{l} \times \vec{r}}{|r|^3} \quad \text{for a charge } q, \text{ with velocity } v;$$


$$\vec{B} = \frac{\mu_0}{4\pi} \cdot q \cdot \frac{\vec{v} \times \vec{r}}{|r|^3}$$

transformed designs:


linkage vs leakage.

core type:

mutual induction

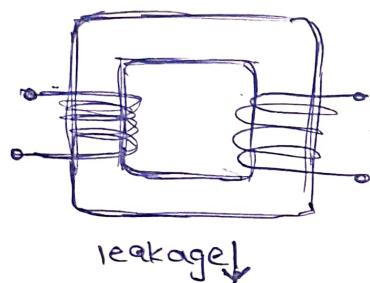

shell type:

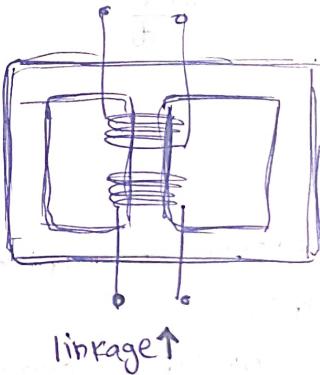

* AC-AC : transformers

AC-DC: rectifiers (via p-n diodes)

- half wave rectifier

- full wave rectifier.

large DC outputs - commutators

DC-DC: DC DC converters

both up & down is possible.

DC-AC: inverters

1) motor → current to work.

2) generator → work to current (AC or DC)

3) inverter → work to current (AC).

↑
current
(DC)

- metals: unipolar transport (e^-)
 - semiconductors: bipolar transport (e^- , holes). } bandgap theory... is the valid one... - read it.
- electronic devices**
- BJT
(bipolar) MOSFET
(unipolar*)
metal oxide semi conductor
field effect transistor.

* drift mobility:

$$V(n) = -\mu(n) * E$$

mobility ($\text{cm}^2/\text{V}\cdot\text{sec.}$)
 - dopant conc. (n or p too!)
 - temperature.

$$\begin{aligned} \mu_e(\text{Si}, 300K) &= 1350 \text{ cm}^2/\text{Vs} \\ \mu_{H^+}(\text{Si}, 300K) &= 450 \text{ cm}^2/\text{Vs.} \end{aligned} \quad \left. \right\} \text{In class...}$$


$$\boxed{I = \sigma \cdot E} \rightarrow \text{Ohms law (macroscopic).} \quad \boxed{\sigma = 9 \cdot n \cdot A}$$

Signal Processing:

- physical world has signals - pressure
 - Temp
 - Light. Analogue.

parameters:

Gain
 Noise
 delay
 Bandwidth
 power.

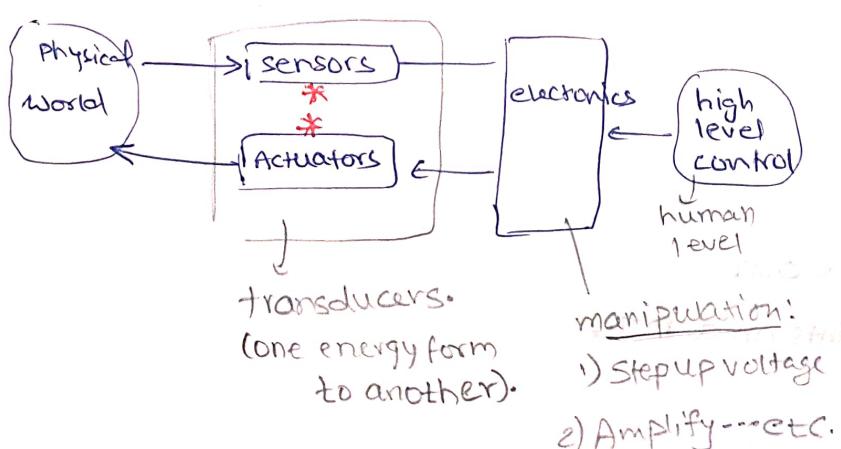

- manipulation:
 1) Step up voltage
 2) Amplify...etc.

* waveforms can be

- timevariant

- transient or periodic.

Sudden burst & falls to zero. Eq: step voltage




Resistors:-

various types.

* Color coding: (resistors are very small).

CCR
Carbon ... resistors

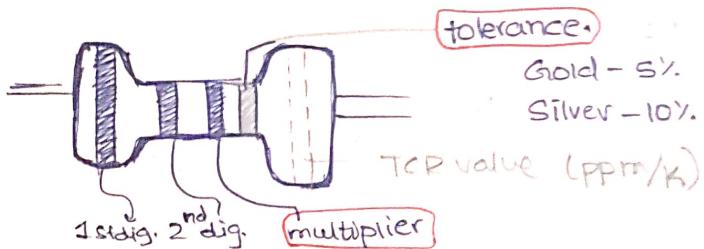- powder of graphite & ceramic insulator
- no inductance.



Black 0 $\times 10^0$

Blue 1 $\times 10^1$

Red 2 $\times 10^2$

Orange 3 $\times 10^3$

Yellow 4 $\times 10^4$

Green 5 $\times 10^5$

Blue 6 $\times 10^6$

Violet 7 $\times 10^7$


Gray 8 $\times 10^8$

White 9 $\times 10^9$

* Gold $\times 10^{-1}$ 5% tolerance

* Silver $\times 10^{-2}$ 10% tolerance.

* zero ohm resistor:

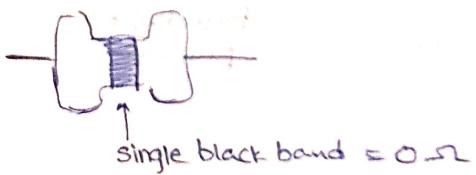

* connects two points on a PCB.

* variable resistors:-] Work as sensors.

1) LDR:

light-dependent resistor.


(as light $I \uparrow, R \downarrow$)

1) Rheostat: (1a)

2) potentiometer.

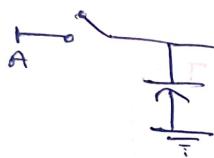3) switched capacitor circuit: (has no resistor;

- tunable over large range. but follows : $V = IR$ rule)



} but these are not the usual mechanical switches & capacitors

frequency is KHz

plastic switches break!

- MOSFET capacitor : $1\text{ pF} - 1\text{nF}$
- MOSFET Switch [transistors] : OFF - resistance in $1\text{G}\Omega$.
ON - resistance in $0.1\text{k}\Omega$.

Switching frequency : $10\text{ Hz} - 10\text{GHz}$
(audio) (radio)

$$\therefore (I_{AB} = f \cdot C \cdot \Delta V)^*$$

$$\therefore R = \frac{1}{f \cdot C}$$

f range: $10\text{Hz} - 10\text{GHz}$.

$$C = 100\text{pF}$$

$$\therefore R_{eff} \rightarrow 1\text{k}\Omega - 1\text{G}\Omega$$

→ characteristics:-

- 1) Power rating: amount of power; can be dissipated for an indefinite period, without degrading its performance.

large size → higher Power rating.

$$I_{max} = \sqrt{\frac{P_{max.}}{R}}$$

2) TCR: temp. coeff ...

$$R = R_0 (1 + (T - T_0)\alpha)$$

+ve TCR : metals. $T = U \cdot nq$

→ decreases.

[PTC]

* Thermistor: Temp. sensing. (so high TC).

negative temperature coefficient :-

(semiconductors)

R decreases as
T increases.

μ_b but $n \uparrow \uparrow$

$\therefore \sigma \uparrow$.

$$\sigma = q(N_e + n_p \cdot \mu_p)$$

* Heavily doped silicon :-

n^{++} -Si] behave like metals.
 p^{++} -Si] PTC ✓

* So; there must be a doping; for zero TC.
i.e. $\mu_b = n \uparrow$

* manganin, constantine. ≈ 0 TCR material.

Capacitors:-

Farad.

$$C = \frac{Q}{V}$$

electric field


$$\frac{1}{2} CV^2$$

$$C = \frac{dQ}{dV}$$

dynamic capacitance.

parallel space:-
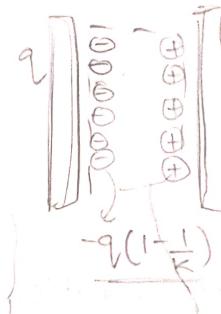
$$C = \frac{\epsilon_r \epsilon_0 A}{d}$$



$$C = \frac{q}{V}$$

∴ Now, Store more charge ($k \cdot q$)

for same voltage.


* Capacitors can be used to store information...

DRAM (Digital, MOSFET based)

CCD (analog)

(charge couple device).

* Used as humidity sensor :-

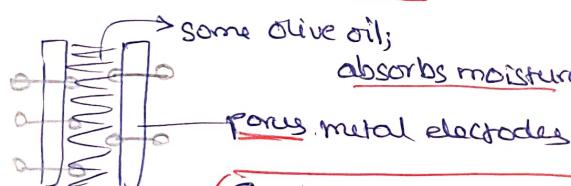

Er charges, when water added.

Inductor: $1 \text{ NH} - 1 \text{ H}$

(Henry).

magnetic field

$$\frac{1}{2} L i^2$$
$$\text{Emf} = -L \cdot \frac{di}{dt}$$

* To boost inductance, use magnetic core - iron.

* Coupled with capacitors, to have RF resonators.

radio frequency.

Wave forms & signal processing:-

[SNR]: Signal to noise ratio.

) goes on getting better.

* Circuits involved in manipulating signals:-

amplifiers

filters

rectifiers

inverter

a logic gate

a DC to AC.

} all will be studied in subsequent section of EE101.

Transducers:

convert signed to non EEE & viceversa

actuators

Peltier cooler.

(gives ΔT wrt ΔV)

sensor


thermocouple.

(gives ΔV wrt ΔT)


* **Analogue:** continuous wrt both value in y-axis
signal

time (x-axis)

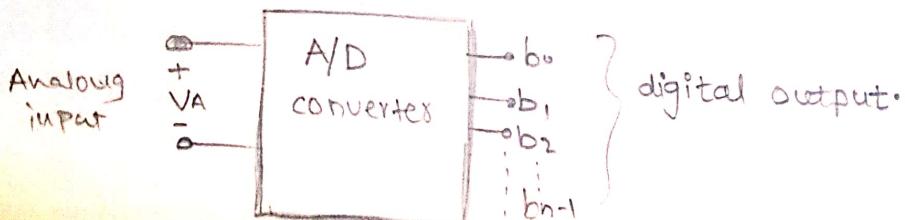Digital: quantized (wrt y-values) as well as sampled at discrete points in time.




For e.g:-

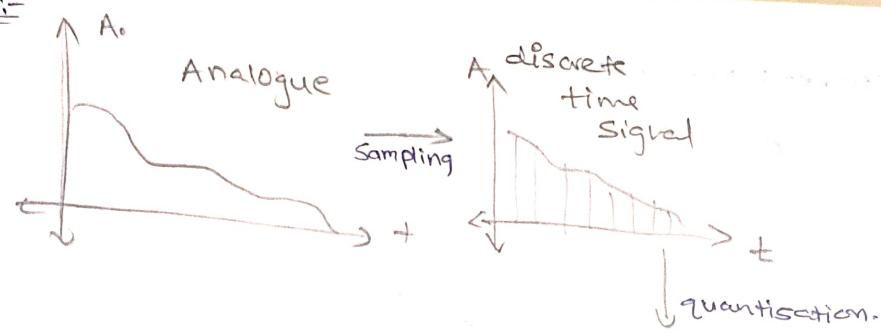

digital doesn't mean binary.

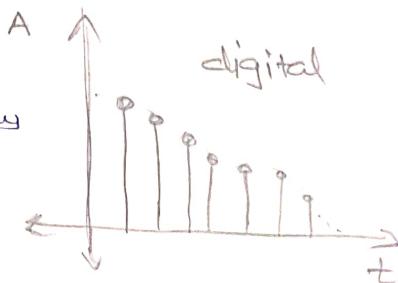binary is just most famous form for digital signals.




* Representing Source (transducer) in circuits :-


- How are signals represented?

A) Thevenin form:- voltage source (V_s) with series resistance R_s (preferably, when R_s is low; ideally zero).

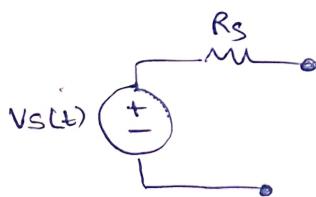B) Norton form:- current source (i_s) with parallel resistance R_p . (preferably, when R_p is high; ideally ∞).



Thevenin

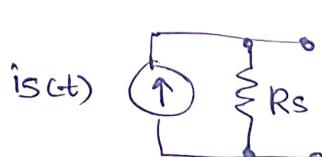

Norton.

* Noise sources / External: cross talks; capacitive coupling, industrial noise, from space.


/ Internal: thermal noise (random thermal motion of e, h, t); Avalanche noise; generation-recombination noise.

flicker noise ($\frac{1}{f}$ noise)


* Noise mitigation techniques:-, Notch filter @ 50 Hz (analog noise mitigation)
reducing the Severity of something.

* Frequency response: notch filter.
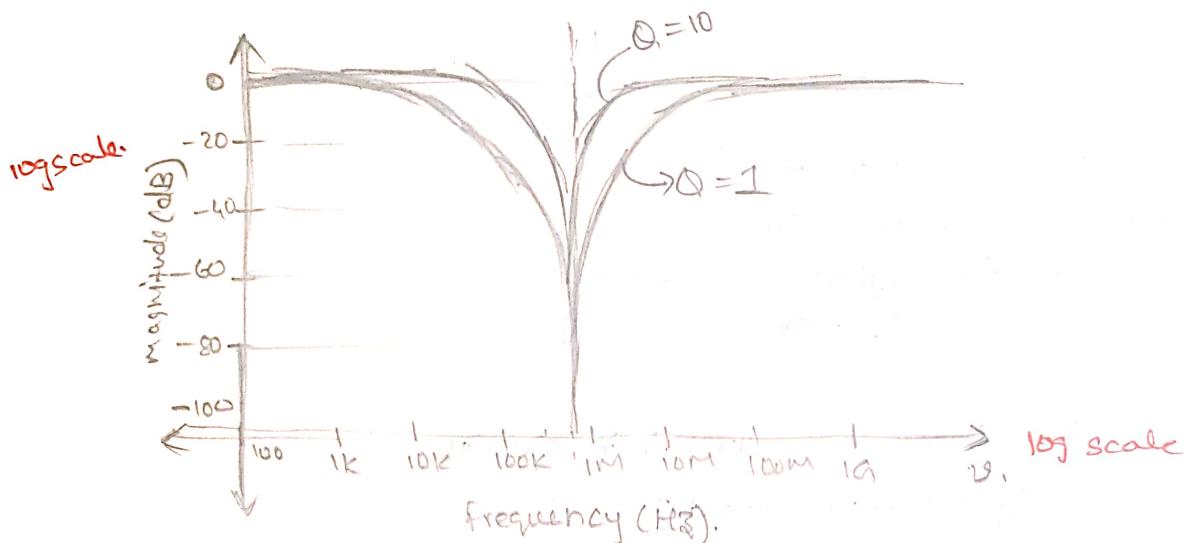
$$\therefore \text{Quality factor } Q = \frac{f_n}{\Delta f}$$



Opposite is RLC resonator:-

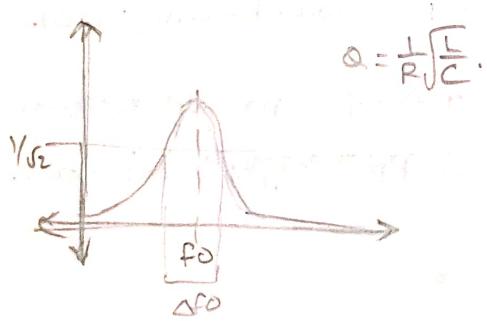

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

3) Impu

4) ramp



5) exp.

VCA

waveforms: signals; vary with time.

1) periodic or transient:




2) composite waveforms:

$$y = e^{-t} \sin x$$

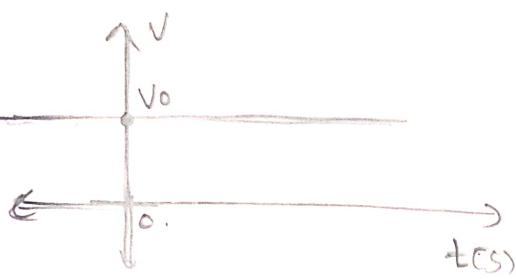
3) DC signal:

$$V(t) = V_0 \text{ for } -\infty < t < \infty$$



3) impulse wave form:


$\delta(t)$ → unit waveform-impulse

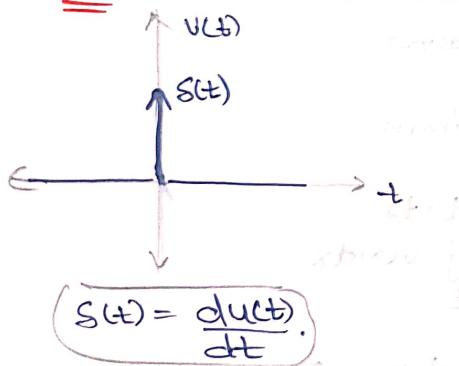

($S(t) = \frac{d u(t)}{dt}$)

4) ramp function:

$r(t)$ unit ramp function

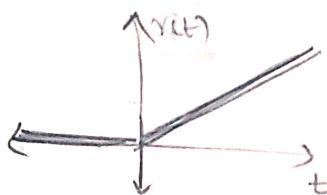

$$r(t) = \int u(t) dt$$


$r(t) = t$ (numerically).

unit step
unit impulse
unit ramp } singularity functions.

5) exp. decay:

$$v(t) = V_A e^{-t/T_C} u(t)$$

T_C → time constant.

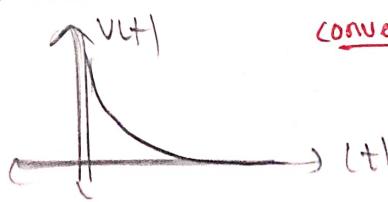

convention:

signal goes to '0' after $5T_C$.

6 • sinusoidal waveform:-

$$V(t) = V_A \cdot \sin\left(\frac{2\pi}{T_0} \cdot t\right)$$


2 parameters... +1, initial phase.
(or time shift)

frequency $f_0 = \frac{1}{T_0}$

$$\omega_0 = 2\pi f_0$$

- Power $\propto V_A^2 \checkmark$ (do $\int V^2 dt$ & check!)
- Power $\propto \omega_0^2 \times$.

7) composite waveform:-

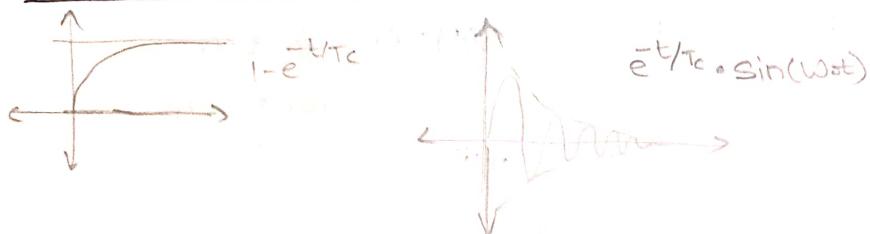

waveform - partial descriptors:-

- characterize important features of a waveform; but not complete waveform.

categories:-

Temporal features:- (time related.)

- A signal $V(t) = V(t+t_0) \neq t$
 t_0 is small.
signal is "periodic".
to - period

- $V(t)$ is causal if there exists T ; s.t. $(V(t)) = 0$ for $t < T$

(if $t < T$)

($t > T$)

reality na!

Amplitude features:-

$V_{PP} = V_{max} - V_{min}$.

$$V_{avg} = \frac{1}{T} \cdot \int_t^{t+T} V(x) dx$$

$$V_{rms} = \sqrt{\frac{1}{T} \cdot \int_t^{t+T} (V(x))^2 dx}$$

$$\text{avg. power to resistor} = \frac{V_{rms}^2}{R}$$

consider what voltage

value to consider?

DC part

DC components:-

1) Switches!

MOSFET switch. $10\text{k}\Omega$ to $10\text{G}\Omega$.

.....

2) Volt source:


ideal:

also


$$R_s = 0.$$

(since

vertical
slope).

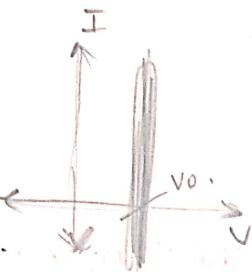

Practical:

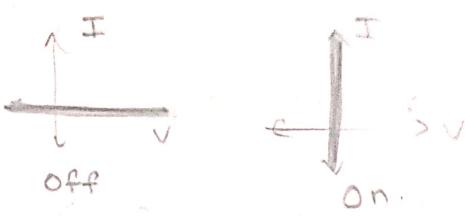

Eg: transducer. (Temp \rightarrow V_s).] time variant

Battery.

] time invariant.


3) Current source:

ideal




Shunt resistance = $\infty \Omega$.
//el connection.

Eg: Solar cell.

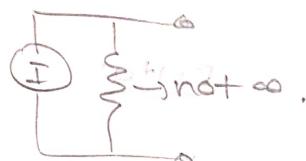


* Switch off action: may ask dumb-tricky questions....

1) Voltage source.

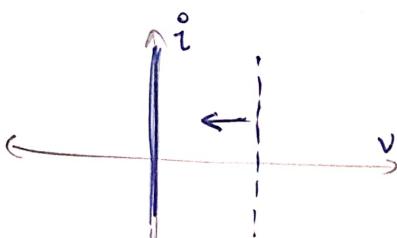

\therefore replaced by
short circuit.

2) Current source.

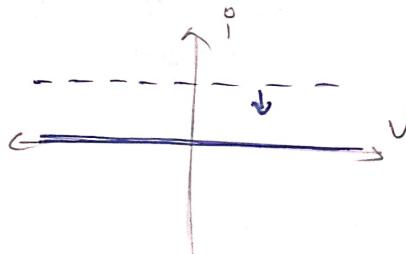


replace by
open circuit.

voltage divider:-

- When output voltage is fraction of input voltage.

1) Resistive (R-R)

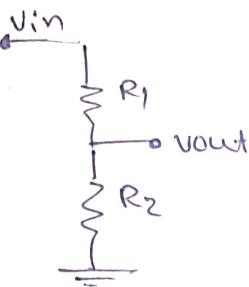

$$V_{out} = \frac{R_2}{R_1 + R_2} \cdot V_{in}$$

2) Transformers (L-L) (for AC-AC)

3) Filters (R-C, R-L, RLC)


} offer voltage division; in frequency selective manner.

current divider :- current bypass.

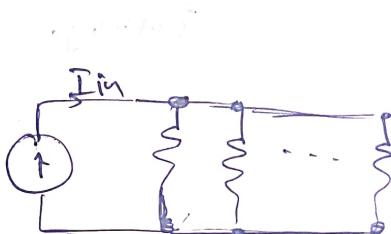1) Shunt resistors

$$I_x = \frac{G_x}{\sum G_x} \cdot I_{in}$$


$$\text{or } I_x = \frac{Y_{Rx}}{\sum Y_{Rx}} \cdot I_{in}$$



Circuit Transformations:- (Results are in impedance-Z)


- Similar algebra to R resistors

Delta:

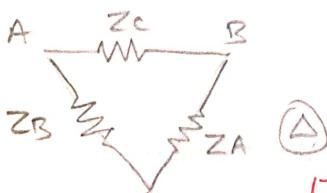


$$Z_1 = \frac{Z_B \cdot Z_C}{Z_A + Z_B + Z_C}$$

& cyclic.

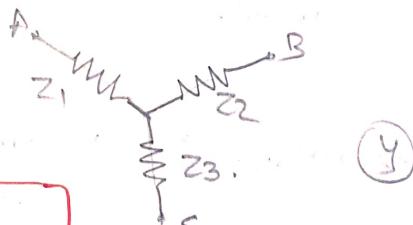


Star:

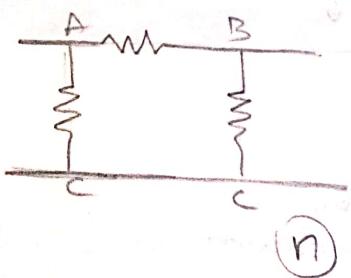→ Proof: compare coefficients as true & V_A, V_B, V_C




$$Z_A = \frac{\sum Z_{i2}}{Z_1}$$


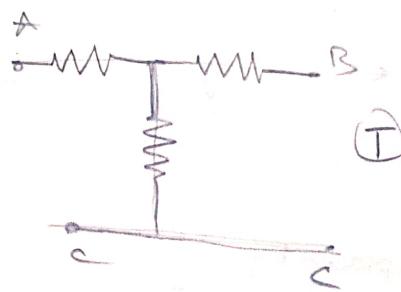


PV cell:-

* diode characteristic:-

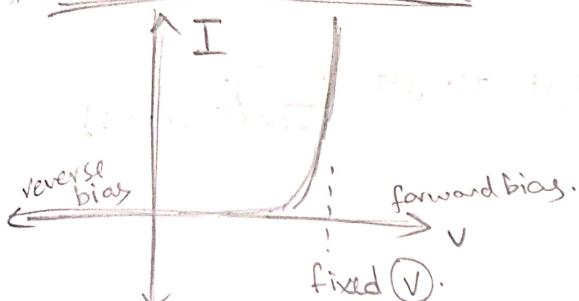


When light is shine,
in PV cell:

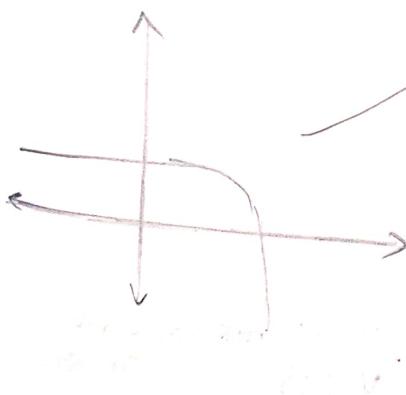
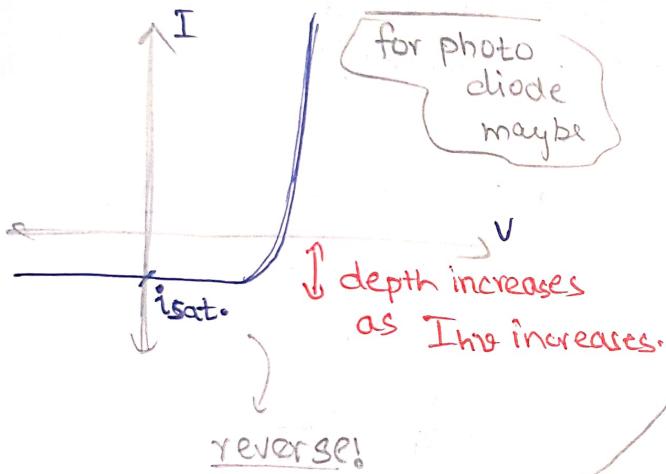


→ Solar cell:

→ photo-Voltaic cell:-

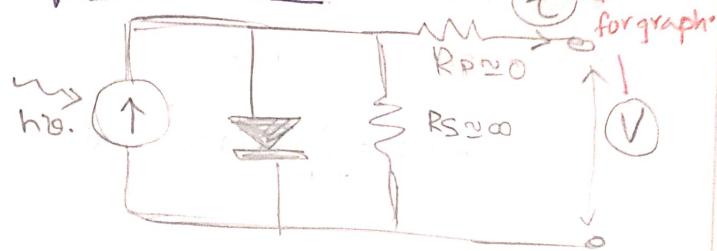

IV characteristic is:-

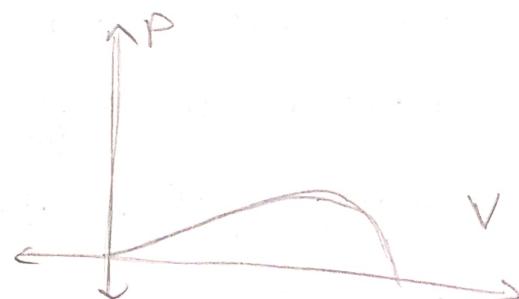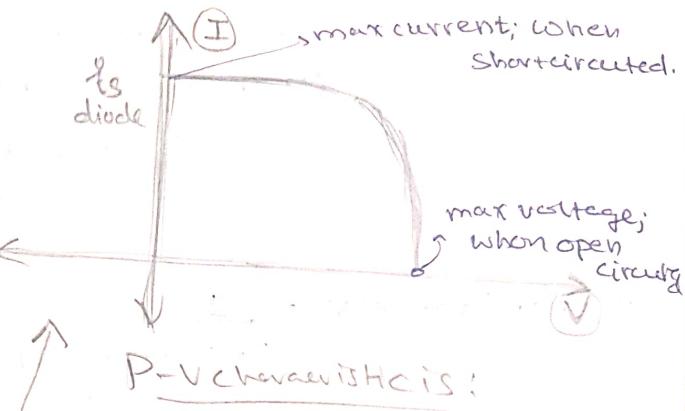

(think once more!)

photovoltaic cell

maximum power point

maximum efficiency



→ S-domain Circuit analysis:- (AC inputs)

• We write impedances for R, L, C.

• We apply Fourier transformation on $V_s(t)$ to get $V_s(s)$.

$$V_s(s) = \int_{-\infty}^{\infty} V_s(t) \cdot e^{-st} dt \quad \text{or} \quad V_s(s) = \int_0^T V_s(t) \cdot \sin(st) dt$$

complete!

coefficients!

physical world! ...

& $V_s(t)$ is an odd periodic function of period T.

• All the laws & equations, applicable to $V_s(t)$ are also true for a $V_s(s)$

$$\because V_s(s) = V_s \cdot \sin(st + \phi)$$

& since, E is a linear law field,
superposition works!

* Admittance (Y) = $\frac{1}{\text{Impedance } (Z)}$

* Resistance (R) $\rightarrow \frac{Z}{R}$

capacitance (C) $\rightarrow \frac{1}{j\omega C}$ or $\frac{1}{sC}$

Reactance (L)
(Inductance) $\rightarrow L \cdot j\omega$ or sL

Assumption: causal systems:-
 $V_C(0) = 0$
 $\dot{V}_C(0) = 0$.
 $V_S(0) = 0$.
 $i_L(0) = 0$.

* Impedance in series.

$$\sum Z_i = Z_{\text{net}}$$

parallel

$$\sum \frac{1}{Z_i} = \frac{1}{Z_{\text{net}}}$$

→ Wave form transformations:-


<u>V_s</u>	<u>$V_s(t)$</u>
impulse	$\delta(t)$
Step	$u(t)$
ramp	$t u(t)$

coefficients for each $\sin(st)$

$$\frac{1}{V_s(s)}$$

$$\frac{1}{s}$$

$$\frac{1}{s^2}$$

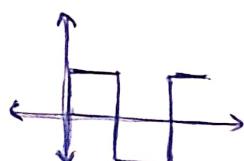

$$\frac{4V}{\pi} \cdot \frac{1}{s} \text{ for } s \text{ is odd;}$$

$$\frac{4V}{\pi} \cdot 0 \text{ for } s \text{ is even.}$$

etc.

Filters

How to examine frequency response?

Pass a "sinusoidal" wave of frequency ω .

Why?

Because form is conserved.

∴ Frequency is conserved.

* two types passive filters use of R,L,C. No amplification!

→ active filters


has semi-conductor devices: amplification takes place

Amplifier.


↳ defintⁿ of passive filters.

Low pass filter, passive:


ideal:

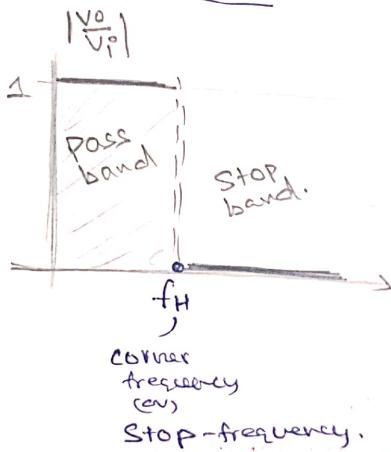

real:

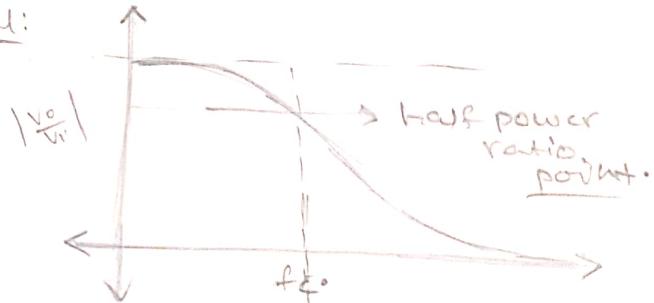

first order LPF & (low pass filter)

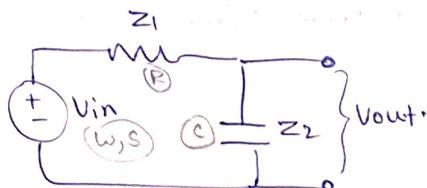

$$V_{out} = \frac{Z_2}{Z_1 + Z_2} V_{in}$$

$$T(s) = \frac{1}{Cs} \cdot \frac{1}{\frac{1}{Cs} + R}$$

$$T(s) = \frac{1}{1 + (RC)s}$$

$$\text{So; power} = Y_2 \rightarrow |T(s)| = \frac{1}{\sqrt{2}}$$

$$\therefore \frac{1}{\sqrt{1 + (PC\omega)^2}} = \frac{1}{\sqrt{2}}$$

$$\boxed{\omega_0 = Y_{RC}} = \underline{\text{frequency}}$$

$$T(s) = \frac{1}{1 + \frac{s}{\omega_0}}$$

for physical frequencies; $s = j\omega$.

$$T(j\omega) = \frac{1}{1 + j(\frac{\omega}{\omega_0})}$$


$$|T(j\omega)| = \frac{1}{\sqrt{1 + (\frac{\omega}{\omega_0})^2}}$$

$$\angle T(j\omega) = -\tan^{-1}(\frac{\omega}{\omega_0})$$

$$\omega_0 = \frac{1}{RC}$$

$$\Rightarrow |T(\omega)| = \frac{1}{\sqrt{1 + (\frac{\omega}{\omega_0})^2}}$$

Bode plot:-

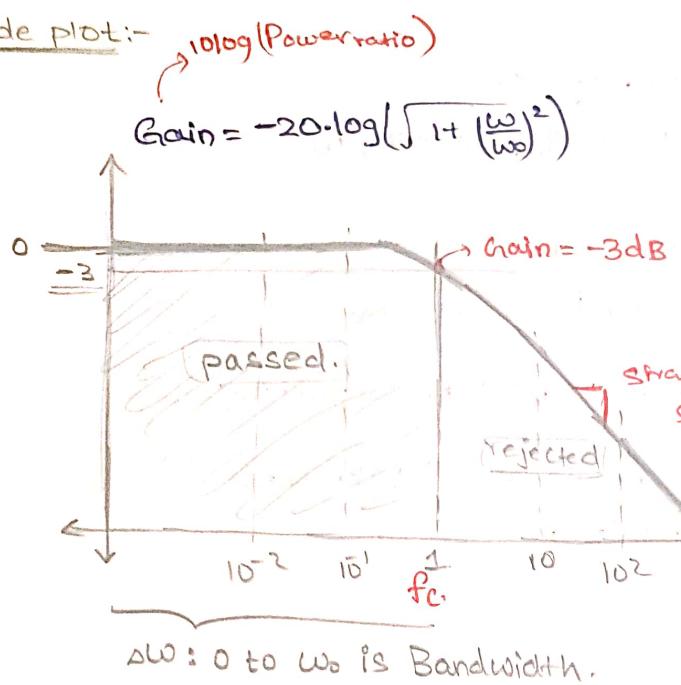


phase is like this.

wrong!

$$G = -20 \cdot \log(1 + \frac{1}{(\frac{\omega}{\omega_0})^2})$$

$G = -20 \cdot \log(\frac{\omega}{\omega_0})$
is a decibel
scale is logarithmic.

$\Delta\omega$: 0 to ω_0 is Bandwidth.

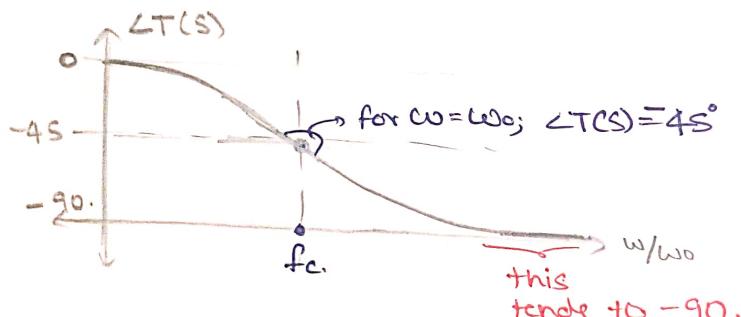

But NOT in Bodeplots!



Gain $\rightarrow -\infty$ (log scale)
as $\omega \rightarrow$ higher & higher.

for HPF:-


$$|T(j\omega)| = \frac{1}{\sqrt{1 + (\frac{\omega}{\omega_0})^2}} \quad \omega_0 = \frac{1}{R} \text{ or } RC.$$

$$LT(j\omega) = \tan^{-1}(\frac{\omega_0}{\omega}).$$

Bodeplots:

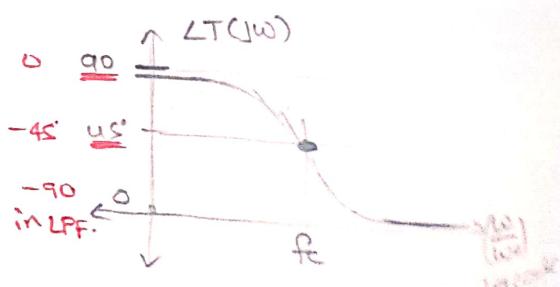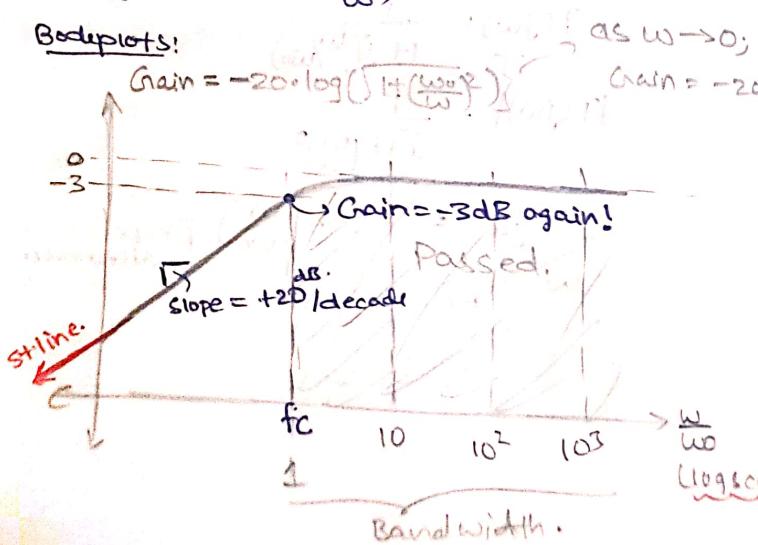

* cascaded LPF:-

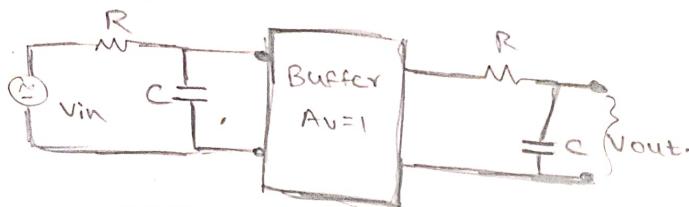


Here; $f_{corner} = \frac{1}{RC}$ (still!) But not half-power point.


$$|T(j\omega)| = \frac{1}{\sqrt{1 + (\frac{\omega}{\omega_0})^2}} \times \frac{1}{\sqrt{1 + (\frac{\omega}{\omega_0})^2}}$$

also; $\angle T(j\omega) = 2 \cdot \tan^{-1}(\frac{\omega}{\omega_0})$.

Bode:

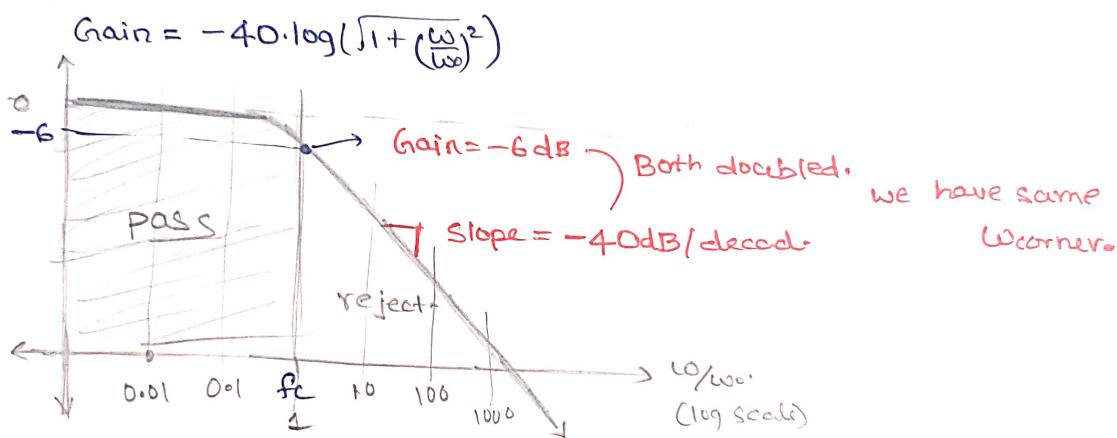

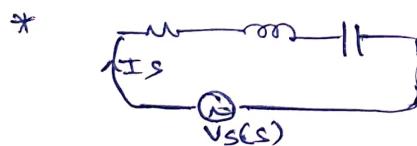
* resonance:- useful as bandpass. / notch filter - stops - bandstop filter;



WE SEE

$$\frac{I_s}{V_s} \text{ or } \frac{V_s}{I_s}$$

Admittance

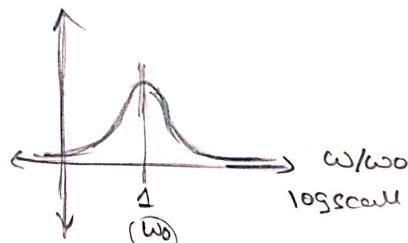


$$|Z(j\omega)| = \sqrt{R^2 + (L\omega - \frac{1}{C\omega})^2}$$

R, L, C, Source in parallel;

$$|Z(j\omega)| \text{ is min for } \omega = \omega_0 = \frac{1}{\sqrt{LC}}$$

$$|Z(j\omega)| = \sqrt{R^2 + \frac{L}{C} \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)^2}$$

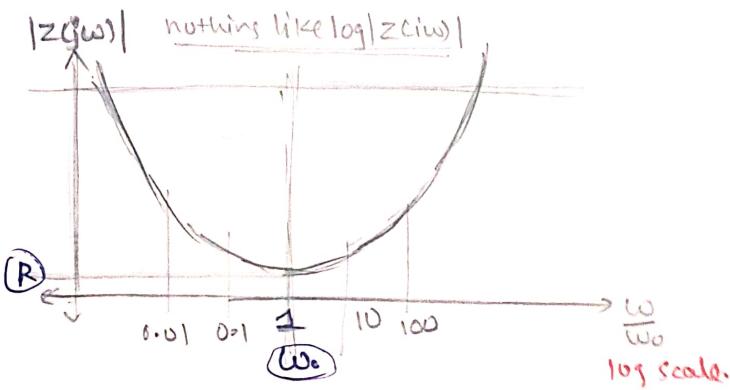


Week-2!

* In a circuit;

N nodes $\rightarrow (N-1)$ independent KCL eqns

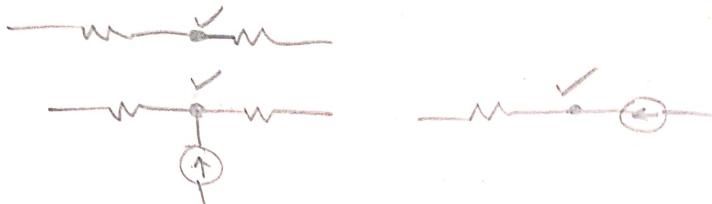node means; connection point of 2 or more elements.



E two terminal devices $\rightarrow (E-N+1)$ independent KVL eqns.

Node-voltage analysis: KCL derived.

1. N -nodes: 1 - reference node [E]; potential = 0.

$N-1$: v_1, v_2, \dots, v_{N-1} voltage values.

circuit variables are voltages.

2. write KCL at $N-1$ nodes. (using I-V constraints) Node

$N-1$ equations for $N-1$ variables (v_1, v_2, \dots, v_{N-1})

3. write matrix. (comes symmetric) \rightarrow marks are given for this.

* N-V analysis, preferred when parallel circuit elements.

$(N-1)$ is small no.

(current source plural circuits)


mesh current preferred when series circuit elem.

divided into many.

($E-N+1$) small no.

voltage source plural circuits

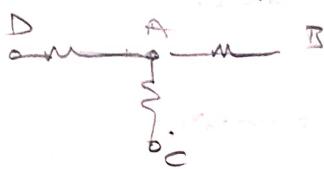writing $\sum V_i (\frac{1}{R_i}) = 0$ by inspection:-



$$V_A + i(\sum \frac{1}{R} \text{ between } A \& \text{ others})$$

$$V_B - i(\sum \frac{1}{R} \text{ between } B \& A)$$




$$V_C - i(\sum \frac{1}{R} \text{ ---})$$

$$V_D - i(\sum \frac{1}{R} \text{ ---})$$

* Voltage-source; is an exception in this approach.

= Source transform to current source; OR write $V_A - V_B = iV$ eqn

Note: source transformation:-

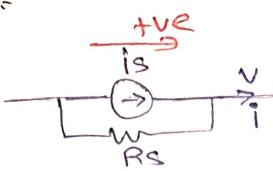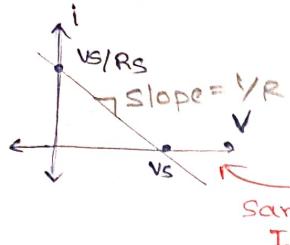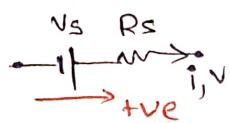


$$V_s = i_s R_s$$

- Resistances same
- relatⁿ b/w V_s, i_s is easy.

for elements; no difference "electrically"
so, we exchange.

→ Mesh current analysis:-

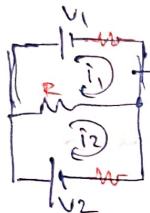

$$V_1 + (i_1 - i_2)R = 0$$

not just i_1, \dots

write absolute current;

following signs as per your

selected directly.

1) E-N+1: mesh current variables

2) write KVL along E-N+1 loops:-

E-N+1 variables, E-N+1 eqns.

(use I-V characteristics, if needed).

3) write matrix:

(comes symmetric)



By inspection:-

$\sum R_i x_i$ can be written....

* current source is exception in this analysis.

- do source transformation, if possible
- or write $i_K = i_{current\ source}$, as one eqn.
- take eqn on supermesh & write $i_A - i_B = i_s$,
combⁿ of
mesh having
this as
common.

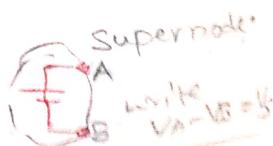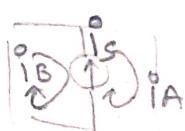(same; super node analogy in N-V-analysis)



→ superposition:-

1) mark all current sources; voltage sources.

2) switch on - S_i ; switch off - remaining all.

\checkmark if $V = V_s$ - if voltage-source; short circuit!

$$V = V_s \quad V = 0$$

if i -source; open circuit!

$$i = i_s$$

$$i = 0$$

3) determine $X/P(S_i)$

switch off.

4) finally; add all; $X = \sum X/P(S_i)$

X can be current; can be voltage difference...
but not Power \rightarrow nonlinear.

* Superposition; applicable to circuits comprising of linear circuit elements.
 $\&$ thus
Source transform.

* Our switch \rightarrow active switch

(we control)

- mechanical,

or

voltage operated. } MOSFET

diode \rightarrow passive switch. " switches.

Self deciding.


- Resistor
- Capacitor
- Inductor
- i -source
- V -source

→ Source circuit, effective representation:-


Thevenin circuit rep.

Norton circuit rep. } independent of load - linear or non-linear.

*

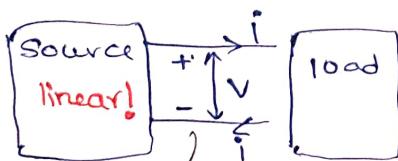

i ; v graph will be

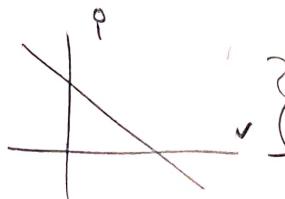

} should mimic
by using

"effective resistor"

{
"effective v-source"
(Thevenin)

| "eff. i-source"
(Norton)

How to proceed:-

1) make load as open.

$$V = V_{\text{Thevenin}}; i = 0.$$

2) make load short circuit;

$$i = i_{\text{Norton}}; V = 0.$$


$$3) R_T = \frac{V_T}{i_N}$$

3) also can calculate; R_T by look-back:

(i.e. switch off all V -sources, i -sources)

& calculate R_{eff} .

* Linear Load:-

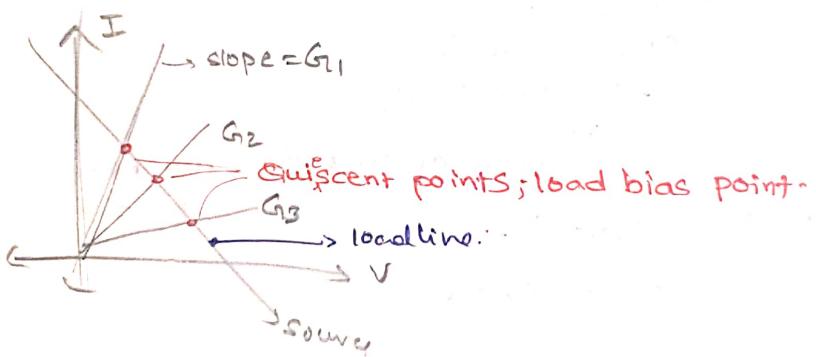


* maximum power transfer:-

\checkmark

Applications:-

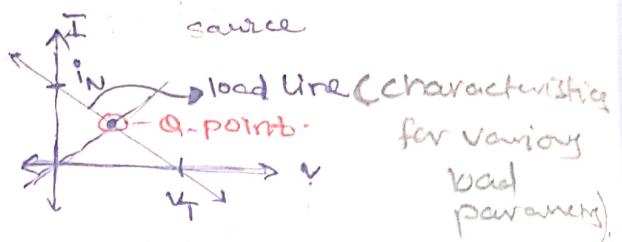- 1) communication systems
- 2) Speaker.
- 3) car ignition.



Week-3:-

- semiconductors, means;

σ or ρ values intermediate.

metal	$\sigma: \text{Si units}$ $> 10^2$
Semicond.	$10^{-6} - 10^5$
insulator	$< 10^{-10}$

→ EEE properties of Silicon:
(electrical & electronic engineering).

$$n_e = 1350 \text{ cm}^2/\text{Vs} \quad \sigma = 0.3 \times 10^3 \text{ S m}^{-1}$$

$$n_h = 450 \text{ cm}^2/\text{V.s}$$

$$E_g = 1.1 \text{ eV}, \quad K = 11 \quad (\text{dielectric constant})$$

→ thermal properties:-

→ optical properties:-

→ mechanical properties:-

* $n_i = n = p$ (pure silicon)

↳ no. of free e^- , h^+ in unit volume
of intrinsic semicond.

$$B = \text{some parameter} = 7.3 \times 10^{15} \text{ cm}^3 \text{ K}^{-3/2}$$

for Si

$$T = \text{temp (K)}$$

$$E_g = \text{band gap energy} = 1.12 \text{ eV for Si}$$

$$k = 8.62 \times 10^{-5} \text{ eV/K.}$$

at 300K

$$n_i = B \cdot T^{3/2} \cdot e^{-E_g/2KT}$$

$$P = n = n_i$$

* doping: intentional introduction of impurities, to change carrier concentrations.

$$N_{\text{impurity}} \gg n_i$$

$$10^{12} - 10^{20} / \text{cc} \quad 10^{10} / \text{cc}$$

* $N_{\text{majority}} \approx N_{\text{impurity}}$.

$$N_{\text{minority}} = \frac{n_i^2}{N_{\text{majority}}} \quad (\because \text{thermal equil. between}$$

generation of e^-h^+ & recombination of e^-h^+).

- semiconductor silicon.
- P-N-Diode: (biasing, characteristics)
- Rectification. (diode applications).
- Regulation. (zener diode).

Band-gap model :-

$E_g > 6 \text{ eV}$ insulators: forbidden energy gap.

$E_g = 0$ metals: overlapping valency & conduction band.

Semiconductors:

valence band n filled
cond. band n empty

$$E_g \approx 1 \text{ eV}$$

Si Ge GaAs
intrinsic
semicond.

1) conduction model)

i) At $T=0$; some covalent bonds break
& generate free electrons.

2) Bandgap:-

for $T > 0$; probability there

for excited e^- .

$$* \vec{V}_{\text{drift}} = \mu E \quad \vec{V}_{\text{drift}} = -\mu E$$

for +ve. for -ve.

(as $T \uparrow$, $\mu \downarrow$) \rightarrow vibrating atoms, block paths...

so thus

$$J = q_0 n_0 \mu E$$


$$\therefore J_{\text{semiconductors}} = (q_0 n + \mu t + q_0 n - \mu t) E$$

\uparrow
Semiconductors.

Diode: isolated n or p doped; act as piezo resistors.

* when joined, large density gradient ($10^6/\text{cc}$ vs $10^4/\text{cc}$)
(via doping!) + Temp. will cause n_p to diffuse.

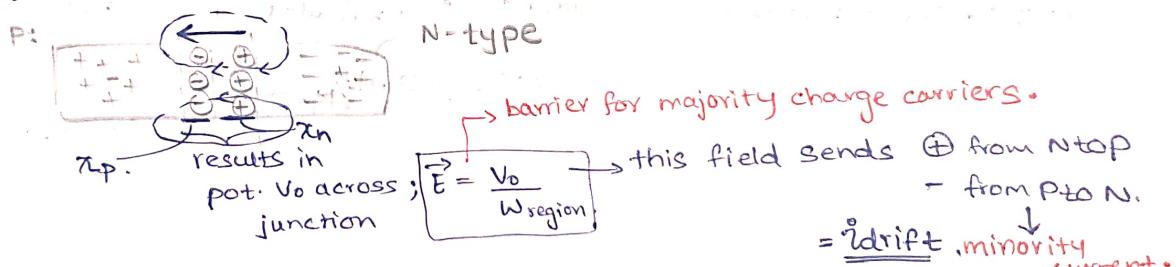* depletion region formed with no free carriers.



* depletion width

$$W = X_n + X_p$$

(fun. of doping conc. in N/P blocks)

$$\rightarrow K \propto P; X_n \propto X_p$$

$$\rightarrow N \gg P, X_n \ll X_p; W = X_p$$

$$\rightarrow N \ll P; X_p \ll X_n; W = X_n$$

* $V_0 = 0.7 \text{ V}$ for Silicon PN.

$$V_0 = V_T \cdot \ln \left(\frac{N_A \cdot N_D}{(N_p)^2} \right); V_T = \frac{kT}{qV}$$

V_T : thermal voltage.

universal defn. of cathode & anode:


* where i flows into terminal; anode.

* where i flows out from terminal, cathode.

& total charge on two surroundings of depletion region:

$$N_A \cdot X_p = N_D \cdot X_n$$

* just

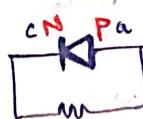

no current ; if light incident on diode; EHP generates; then current \uparrow .

E is separated; due to E in depletion region.

Diffusion current:-

hole diffusion:-



$$J_p = -q D_p \frac{dp(x)}{dx}$$

$$J_n = +q D_n \frac{dp(x)}{dx}$$

$$D_p = 12 \text{ cm}^2/\text{s} \text{ for Si.}$$

$$D_n = 35 \text{ cm}^2/\text{s} \text{ for Si.}$$

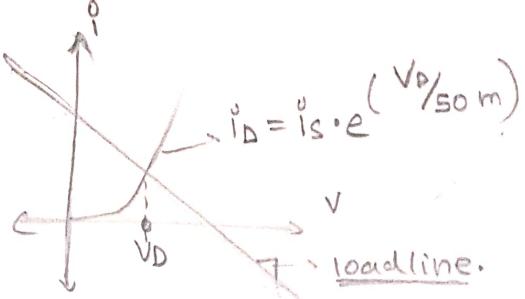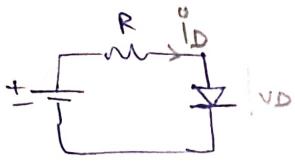forward biasing: + to P-terminal, - to N-terminal



$$R_{\text{dynamic}} = \frac{dV}{di} = \frac{nV_t}{iD}$$

* diode power handling (mA, mW)

$$iD = is \cdot \exp(Vd/nVt)$$

is = scaling current (PA) less.

$$Vt = \frac{kT}{q} \approx 25 \text{ mV at } 290 \text{ K}, \\ n=2.$$

$$\frac{\Delta V}{\Delta T} = -2 \text{ mV/K}$$

is doubles every 10 K rise.

Vt = thermal voltage

$$Vt = \frac{kT}{q}, \\ \approx 25 \text{ mV}$$

- diode capacitance per area:

$$\text{Junction cap} = \frac{E_0 \epsilon_r}{w} \text{ (per area)}$$

- thus; Next charge w changes capacitance.


* temp effect: as T ↑; V_d decreases.

"Varactor" (Signal modulation)

V_d is less; then; can be used as a one way switch.

Schottky diode.

metal semiconductor junction.

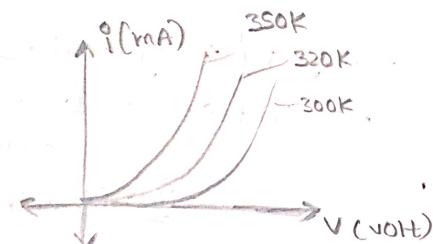


$$\frac{\Delta V}{\Delta T} = -2 \text{ mV/K.}$$

iD is exponential with V_d


$$iD = is \cdot (\exp(Vd/nVt) - 1)$$

Reverse bias:

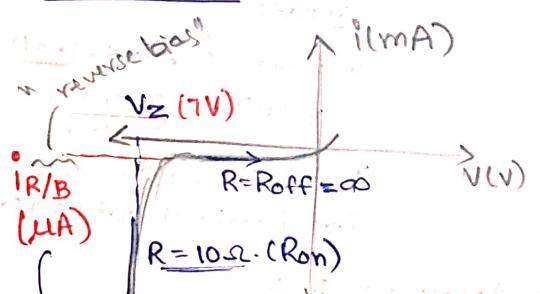

Owing to the minority carriers current.

low leakage current.

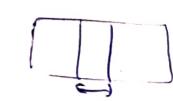

$$W = Ki \sqrt{VR + Vbi}$$

cascade diodes:

P N P N.

high power app (N).

as E increases:

Breakdown #1:-

break bonds.

EHP generated

(Zener effect)

in heavily doped P-N junction or EHP carrier separation.

Breakdown #2:-


accelerated secondary carrier

D (Avalanche effect)
in lightly doped p-n junction.

→ Rectifier circuits

diode - passive switch.

i) diode bridge rectifier, fullwave:-

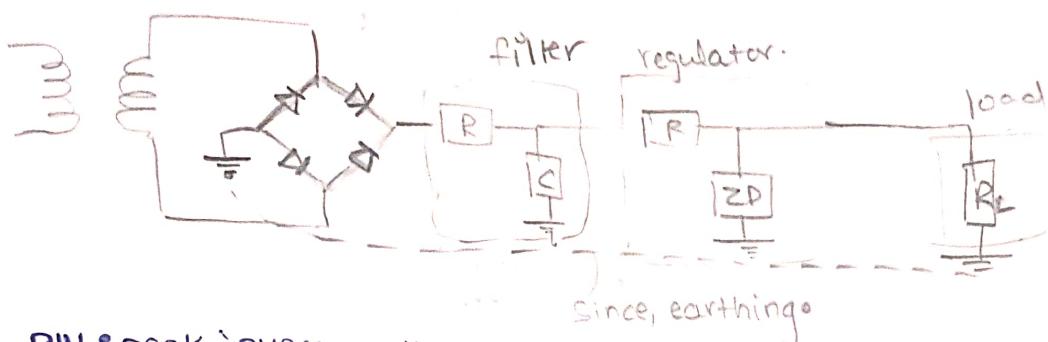

Since, earthing.

PIV : peak inverse voltage.

(for breakdown determination).

* diode:

$V_{bi} = 0.7V$ (ON) → non-ideal, forward bias.


$R_{on} = 0$ (10 Ω is practical)

Reverse: $R_{off} \rightarrow \infty$, $i_{off} = 0$.

ii) half-wave (1-diode):-




> for 1-diode :-

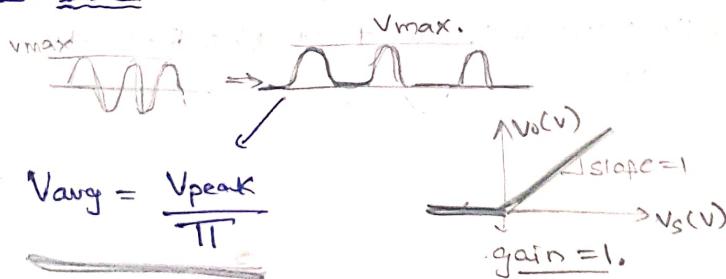


* $V_{avg} = \frac{V_{peak}}{\pi}$

peak inverse voltage ... when diode, reverse biased.

> for 1-diode (2) :-

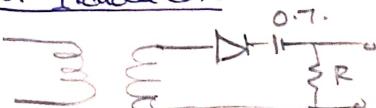


ideal diode model :-

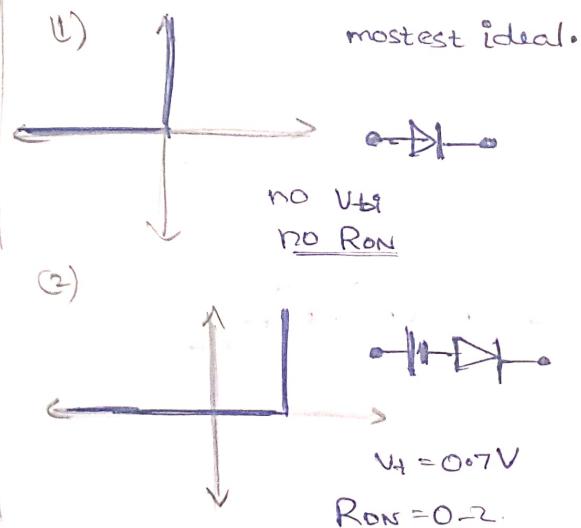

so rectifier waveform.

$$V_{out} = V_{source} - 0.7V$$

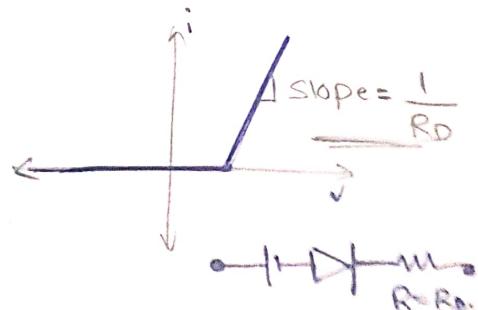* multiple diodes in series; $(2D, 1.4V)$




$$V_{out} = V_s - 0.7 - i_D \cdot R_d$$

P con
mate
easy
high E.

3) Full wave rectifier:-

2 diode

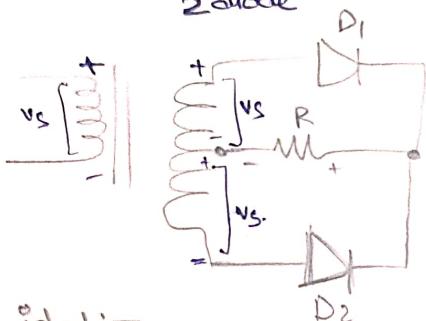


I.D.-1:-

$$* V_{avg} = \frac{2 \cdot V_{peak}}{\pi}$$




$$* PIV = 2 \cdot V_S *$$

since; $V_S + V_S$

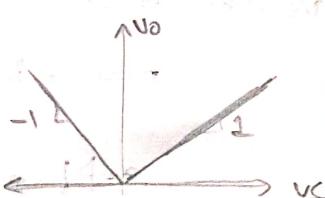

Ideal diode - 2:-

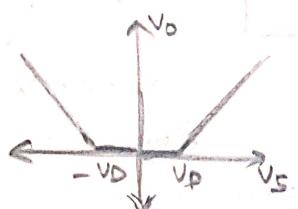


$$V_0 = V_S - 0.7$$

$$PIV = 2 \cdot V_S - 0.7$$

not $2V_S$!

4 diodes :-

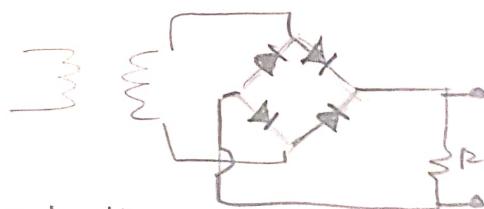

I.D.-1:-

$$V_{avg} = \frac{2 \cdot V_{peak}}{\pi}$$

$$PIV = V_S \text{ damn!}$$

$$V_0 = V_S$$

I.D.-2:-

$$V_0 = V_S - 1.4$$


$$PIV = V_S - 0.7$$

→ Filter capacitor:- / or filter inductor, too!

* smoothing of ripple



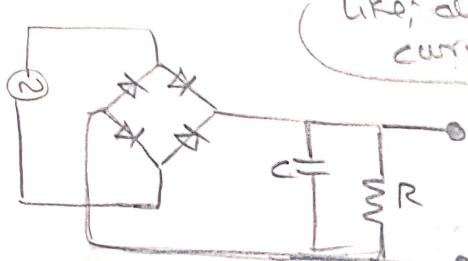* time constant, such that, the R-C. discharge slowly.



Like; diodes will cutoff current; when capacitor tries to discharge?

→ Voltage regulation:
not rectification.

zener diode by:





Aim:

output DC voltage; free from
input (source) fluctuations ($\pm 10\%$)

- reverse breakdown (Zener)
operation.

- constant voltage; over large current range] Hence regulator.

- switch off for low current.

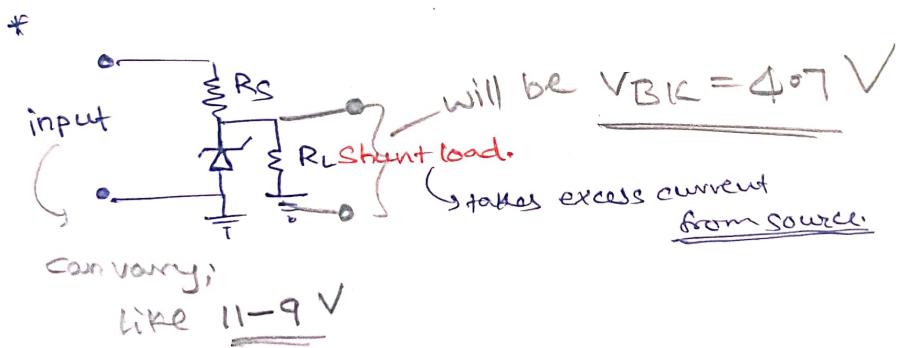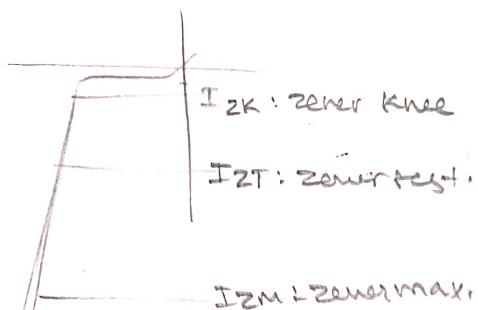

Week-4:-

• Amplifier.

comprises: dependent sources

* so far we've encountered;

passive circuit elements:- R, L, C, diode.
passive!

* transformers are also passive.

$$V_s I_s + V_p I_p = 0 \text{ (transformer eqn)}$$

(Power is same).

* Active circuits \rightarrow signal amplification.

(must have external power supply!)

Transistor (Triode)

> BJT, MOSFET

Amplifier:
- dependent source.
- active circuit.

takes external power

to change signals.

* for AC currents only v_a .

Amplifier circuits include transistors, multiple transistors / or Opamps.

* for cascaded amplifiers;

$$G_t = G(1) \cdot G(2)$$


$$\text{if } G(1) = 20 \text{ dB}, G(2) = 10 \text{ dB}$$

$$G_t = 30 \text{ dB. } (\because \text{dB is log scale}).$$

* 4 kinds:-

VCVS


voltage amp.

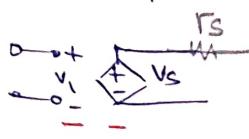

mind the directn.

CCCS

currentamp.

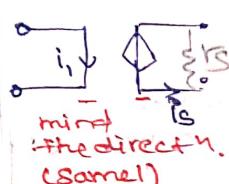


CCVS

trans-resist. amp.



VC CS

trans-conduct. amp.

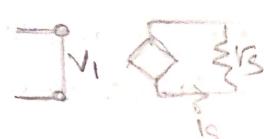

$$*\frac{V_s}{V_i} = A_v \text{ or } \underline{\underline{m}}$$

units are Volt/Volt

$$\frac{i_s}{i_i} = A_i \text{ or } \underline{\underline{m}}$$

amp/amp


$$\frac{V_s}{V_i} = A_R \text{ or } \underline{\underline{m}}$$

ohm




$$\frac{i_s}{V_i} = A_G \text{ or } \underline{\underline{m}}$$

$\underline{\underline{n}}^{-1}$

* Amplifier response:

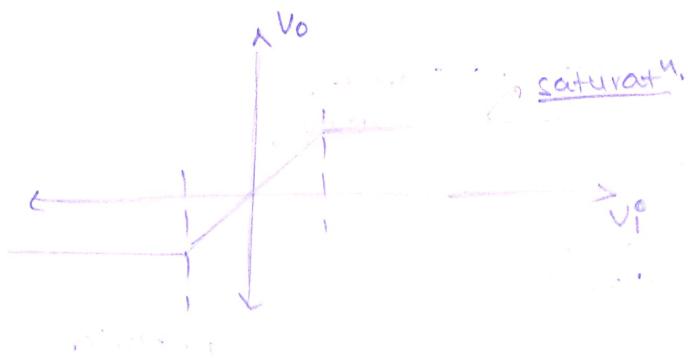

* Transistor β , V_{out} vs V_{in} :

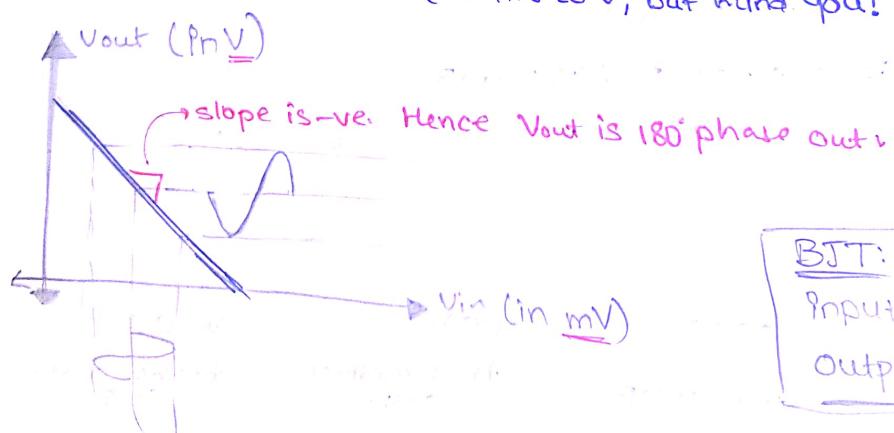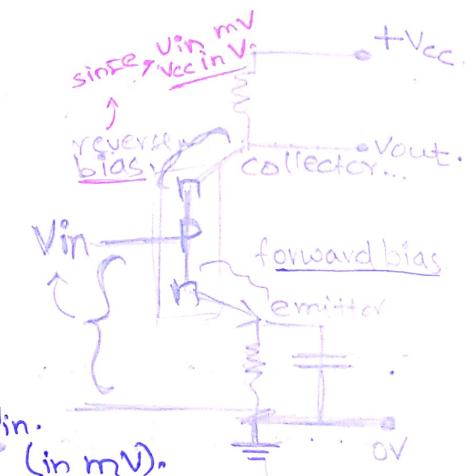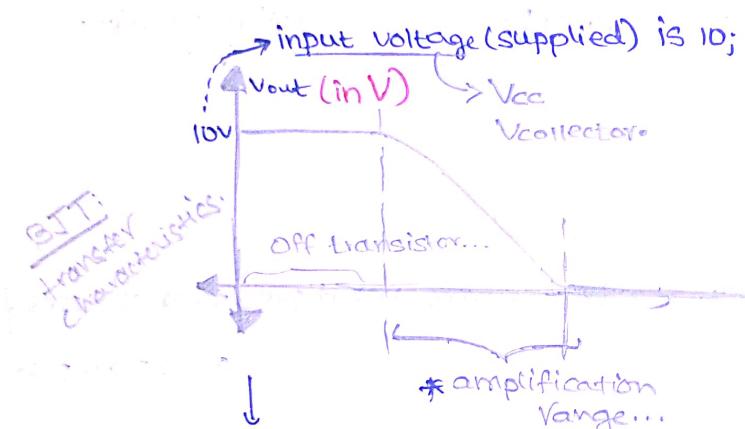

BJT:
Input (B, E)
Output (C, E)

class A amplifiers

only 1 transistor. (npn)


- Linearity is more (so; good match b/w V_{in} , V_{out})
- efficiency is less. (since; always on). transistor.

class-B

2 transistors

(1 npn, 1 pnp)

- less linearity
- more efficiency.

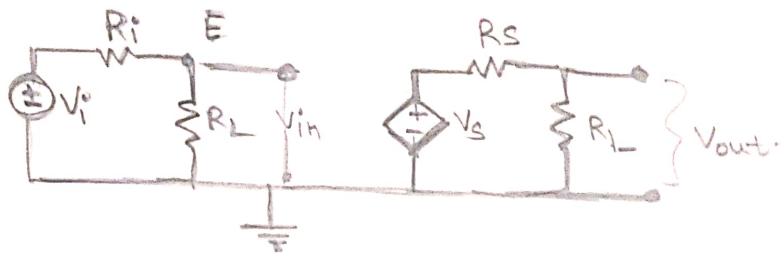

Here; R_i, R_s are real life existances!

don't think why we are keeping resistors unnecessarily!

NOW; we write $V_s = B \cdot V_{in}$


they can't be avoided.

E, find $\frac{V_{out}}{V_i}$ for practical

internal resistances


~~efficiency of amplifier~~
(gain)

Week-5:-

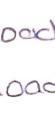
 load as capacitor

 load as inductor.

- 1) * we start by calculating time constant.

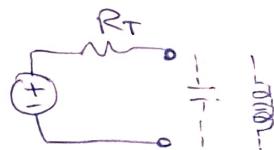- use Thevenin equivalent source.



transient - ST

then; capacitor :- $q = RC$

$$\text{inductor :- } T = \left(\frac{R}{L}\right)^{-1} = \frac{L}{R}$$

2) at $t = 0^-$:

3) at $t = 0^+$: $x_{\text{general}}(t) = x_{t=0^+}(1 - e^{-t/T}) + x_{t=0^+}(e^{-t/T})$

4) at $t = \infty$:

* if $V_{\text{capacitor}} = 0$; short circuited.

$V_{\text{inductor}} = 0$; whatever.

$I_{\text{inductor}} = 0$; open circuit.

Akash! true for any shit!

I think, you wanted to say
"at $t = 0^+$ ".

E_i as $t \rightarrow \infty$: (universal!)

$i_{\text{capacitor}} = 0$


$V_{\text{inductor}} = 0$

equilibrium state.


} for DC. not AC.

inductor doesn't allow abrupt change in i_L ,
capacitor doesn't allow abrupt change in V_C .
(when series connected to resistance)


* for pulse voltages:-

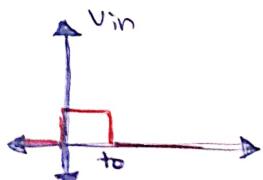

for capacitor:-

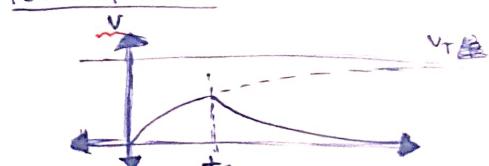


for inductor:-

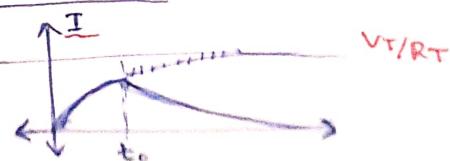

But because of opening/closing switch;
 V_R, i_R could change abruptly.
(change in i_L, V_C)

WEEK - 6:

* equivalent circuit:-

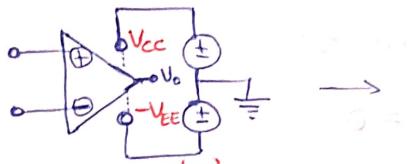


this ± 5 to ± 15 V must be supplied.
(not drawn always).

Here; cascading transistors.

$$V_A \rightarrow \infty$$

$$R_i \rightarrow \infty$$

$$R_o \rightarrow 0$$

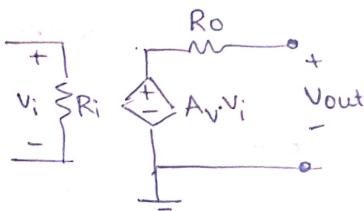

OPAMPS

operational amplifiers.

① → inverting terminal

② → non-inverting terminal.

NOW!

$$(V_+ - V_-) \cdot A_v = V_o$$

Eg for OP-AMPS; $A_v \rightarrow \infty$; called open loop gain.
(cascaded transistors).

$$\therefore (V_+ - V_- \approx 0) \text{ first golden rule.}$$

E_p :

also $R_i \rightarrow \infty$. (typically larger than other circuit resistors)

$$\therefore (I_{in} \approx 0) \text{ second golden rule.}$$


* Note:- • works for AC & DC.

• characteristics of a practical OP-AMP are nearly ideal.


• the DC input power is usually not drawn; But is necessary.

• Broadly; opamps used for two uses.


i) Linear region:

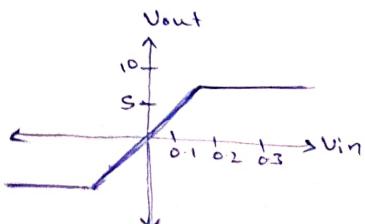

ii) Saturation region:-

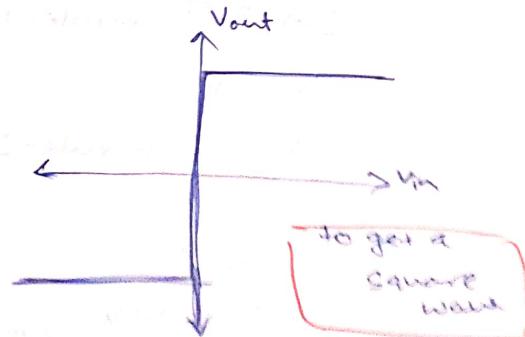

opamp's amplification action:-

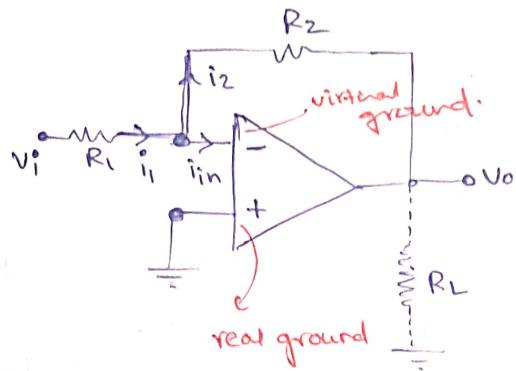

$$\therefore i = i_2$$

$$V_o = -i_2 \cdot R_2$$

$$V_o = -\frac{R_2}{R_1} \cdot V_i$$

∴ inverting amplifier


Golden rule -1:-

$$i_{in} = 0$$

Golden rule -2:-


$$V_- = V_+ = 0$$

in this case

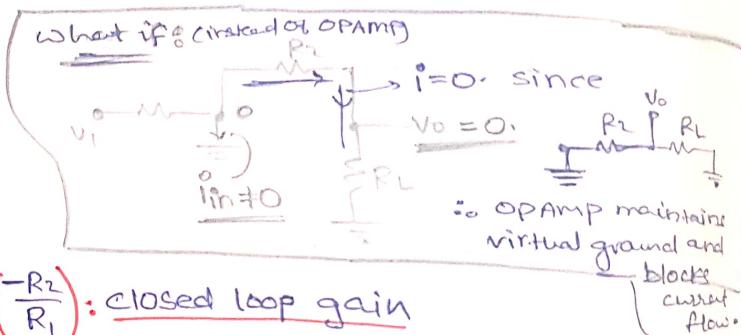

- Here, gain changed by changing resistors;

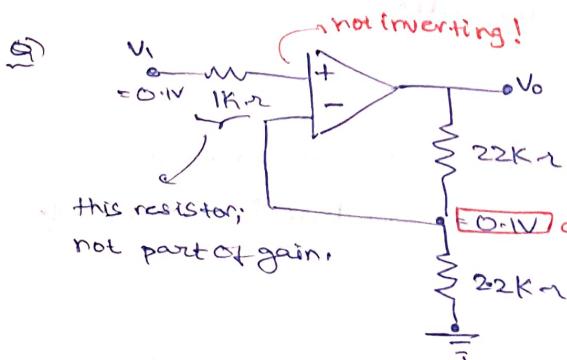- conventional me; gain depends on biasing of transistors.



$$\text{so } i_{in} = 0 \quad \text{G-rule-1}$$


$$\therefore V_+ = V_i$$

$$\therefore V_- = V_i \quad \text{G-rule-2}$$

$$\therefore V_o - 0.1 = 10(0.1)$$

$$V_o = 1.1V$$

+ve ratio

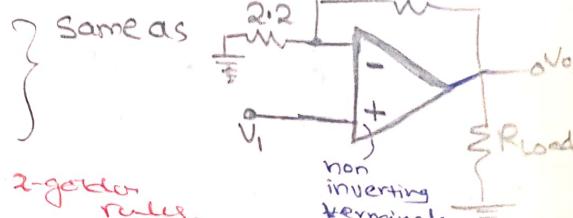

Solid justification
Ground Rules:


$$1) V_+ - V_- \approx 0$$

since V_o is finite
 $A_v \rightarrow \infty$

$$2) i_{in} = \frac{V_+ - V_-}{R_i} \rightarrow 0$$

(non-inverting terminal).

Summer circuit

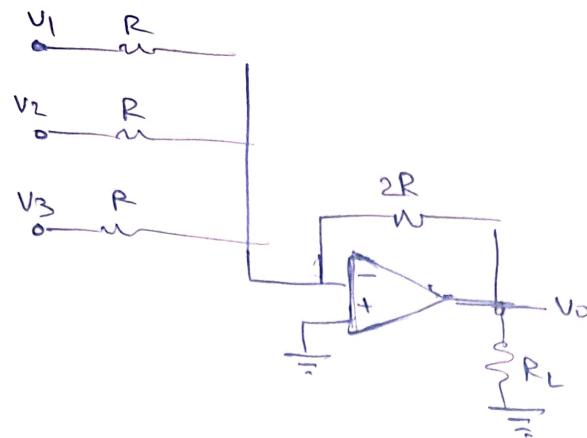

Now:


$$V_0 = -2(V_1 + V_2 + V_3)$$

acting as summer.

- works for DC too.
- think of fourier sum; to generate appropriate input (using AC voltages)

to another circuit.

Where does the current go? -

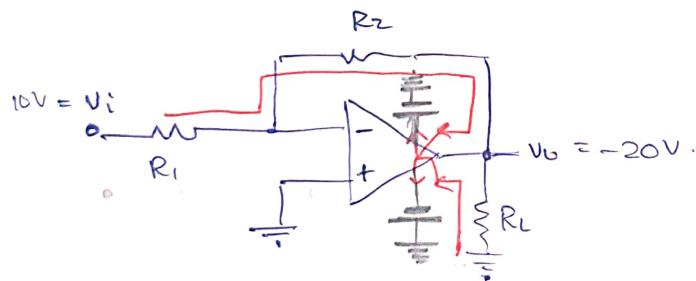

current in red.

Where does the current go?

the V_{CC} ; & V_{EE} ; even though "not drawn all the time".

all still utterly

necessary.

to be present.